

# ***RISC-V Processor Design***

## ***Part 1: The Datapath***



# Outline:

1. Finish up CMOS circuits (nasty realities)
2. How to build a processor

# Nasty Realities: Delays in CMOS circuits

## More physically realistic model:

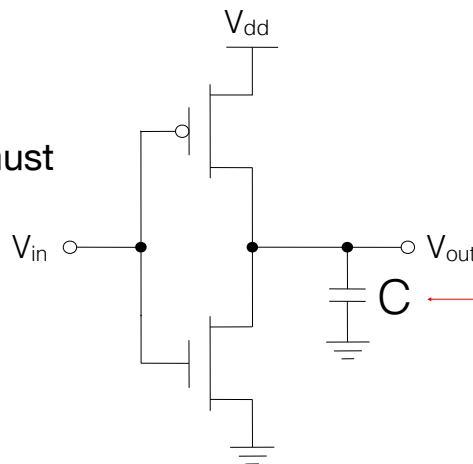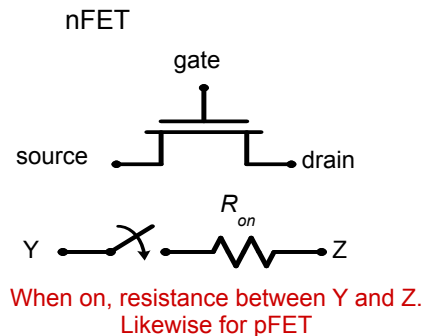1. Transistors are not perfect switches
  - A. They leak when off
  - B. They have finite resistance when on
2. All circuit nodes have capacitance
  - To change their voltage level must displace charge





*Represents the sum of all the capacitance at the output of the inverter and everything to which it connects: (drains, wires, transistor-gate capacitance of next gate(s))*
  
# Transistors as water valves



If **electrons** are water molecules, **transistor resistance** like pipe diameters, and **capacitors** are buckets ...

A “on” p-FET fills up the capacitor with charge.




$$\tau \propto R \cdot C$$

A “on” n-FET empties the bucket.

 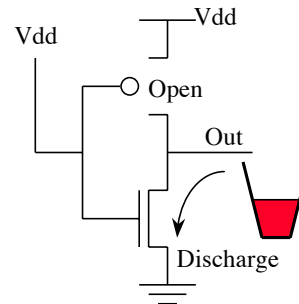

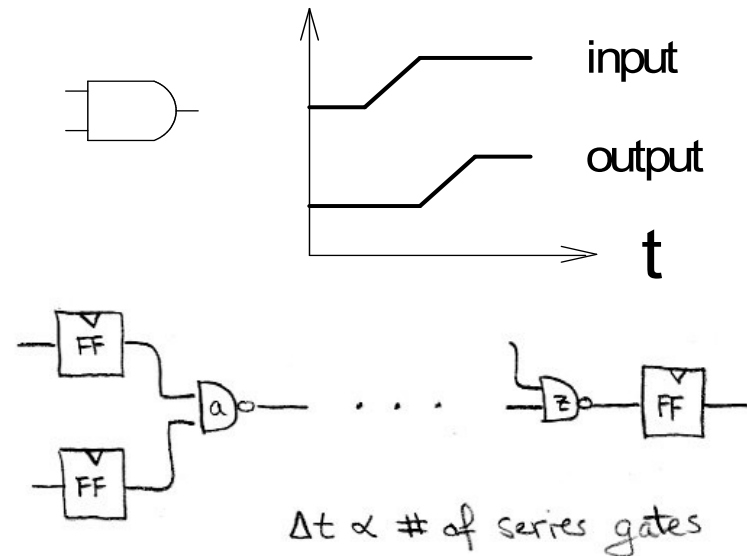
# Consequences

- For every logic gate, delay from input change to output change
- The exact amount of the delay depends on:
  - type of gate, how many other gates it's output connects to, IC process details
- For cascaded gates, delay accumulates
- Remember, flip-flops also have details and timing constraints:  $\tau_{clk-to-q}$  and  $\tau_{setup}$



# Therefore, in General ...

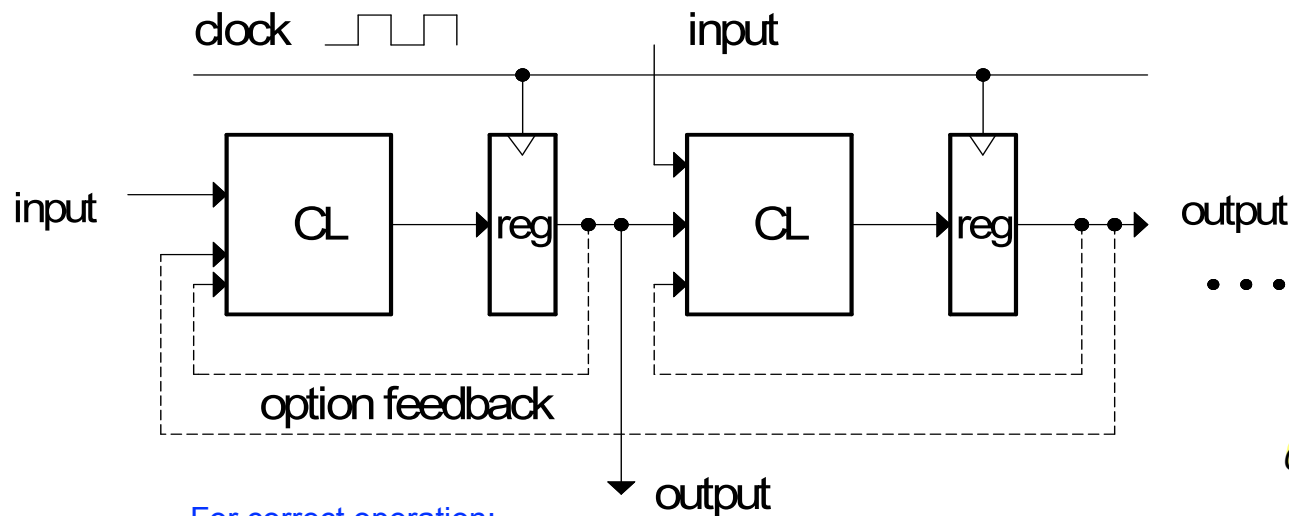

For correct operation:

$$T \geq \tau_{\text{clk} \rightarrow Q} + \tau_{\text{CL}} + \tau_{\text{setup}}$$

for all paths.

*The worst case path is called the “critical path”*

*What can we do to reduce  $T$  (increase frequency)?*

# More nasty realities: CMOS circuits use electrical energy (consume power)

*Energy is the ability to do work (joules).*

*Power is rate of expending energy (watts).*

*Energy Efficiency: energy per operation*


$$P = \frac{dE}{dt}$$

- **Handheld and portable** (battery operated):
  - ❑ Energy Efficiency - limits battery life
  - ❑ Power - limited by heat
- **Infrastructure and servers** (connected to power grid):
  - ❑ Energy Efficiency - dictates operation cost
  - ❑ Power - heat removal contributes to TCO




# Switching Energy: Fundamental Physics

 ***Every logic transition dissipates energy.***



 Models inputs to other gates & wire capacitance





# Chip-Level “switching” Power

$$P = dE / dt$$

$$P_{sw} = 1/2 \alpha C V_{dd}^2 F$$

*“activity factor”, average  
percentage of  
capacitance switching  
per cycle (~ number of  
nodes to switch)*

*Total chip  
capacitance to be  
switched*

*Clock Frequency*

# Reducing power consumption or improving energy efficiency

$$P_{sw} = 1/2 \alpha C V_{dd}^2 F$$

- Power proportional to  $F$ . Can reduce power by reducing frequency. But that doesn't improve energy efficiency (just spreads computation over longer time)
- Energy efficiency:
  - $E_{sw} \propto V_{dd}^2$  but  $\tau_{logic} \propto V_{dd}$  ↙ proportional to
  - Therefore can improve energy efficiency by lowering supply voltage and making up for less performance by using parallelism
  - Main driver of the move towards multi-core processors (Ex: Apple M1 had 8 cores)

# Great Idea #1: Abstraction (Levels of Representation/Interpretation)

```
lw  t0, t2, 0
lw  t1, t2, 4
sw  t1, t2, 0
sw  t0, t2, 4
```

High Level Language  
Program (e.g., C)

*Compiler*

Assembly Language  
Program (e.g., RISC-V)

*Assembler*


Machine Language  
Program (RISC-V)

```
temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;
```

Anything can be represented  
as a *number*,  
i.e., data or instructions


```
0000 1001 1100 0110 1010 1111 0101 1000
1010 1111 0101 1000 0000 1001 1100 0110
1100 0110 1010 1111 0101 1000 0000 1001
0101 1000 0000 1001 1100 0110 1010 1111
```

***We are here!***

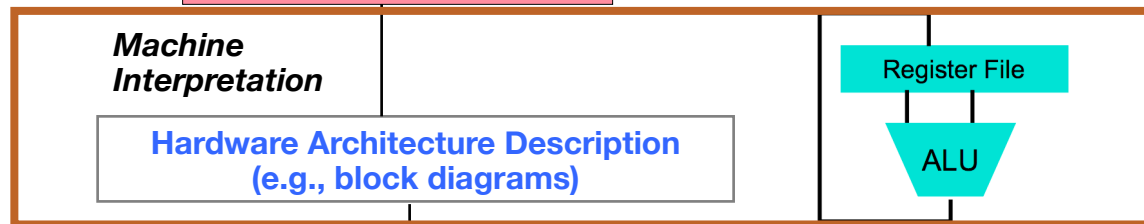

*Architecture  
Implementation*

 Logic Circuit Description  
(Circuit Schematic Diagrams)



# Recap: Complete RV32I ISA

|                       |     |     |     |             |         |       |
|-----------------------|-----|-----|-----|-------------|---------|-------|
| imm[31:12]            |     |     |     | rd          | 0110111 | LUI   |
| imm[31:12]            |     |     |     | rd          | 0010111 | AUIPC |
| imm[20 10:1 11 19:12] |     |     |     | rd          | 1101111 | JAL   |
| imm[11:0]             |     | rs1 | 000 | rd          | 1100111 | JALR  |
| imm[12 10:5]          | rs2 | rs1 | 000 | imm[4:1 11] | 1100011 | BEQ   |
| imm[12 10:5]          | rs2 | rs1 | 001 | imm[4:1 11] | 1100011 | BNE   |
| imm[12 10:5]          | rs2 | rs1 | 100 | imm[4:1 11] | 1100011 | BLT   |
| imm[12 10:5]          | rs2 | rs1 | 101 | imm[4:1 11] | 1100011 | BGE   |
| imm[12 10:5]          | rs2 | rs1 | 110 | imm[4:1 11] | 1100011 | BLTU  |
| imm[12 10:5]          | rs2 | rs1 | 111 | imm[4:1 11] | 1100011 | BGEU  |
| imm[11:0]             |     | rs1 | 000 | rd          | 0000011 | LB    |
| imm[11:0]             |     | rs1 | 001 | rd          | 0000011 | LH    |
| imm[11:0]             |     | rs1 | 010 | rd          | 0000011 | LW    |
| imm[11:0]             |     | rs1 | 100 | rd          | 0000011 | LBU   |
| imm[11:0]             |     | rs1 | 101 | rd          | 0000011 | LHU   |
| imm[11:5]             | rs2 | rs1 | 000 | imm[4:0]    | 0100011 | SB    |
| imm[11:5]             | rs2 | rs1 | 001 | imm[4:0]    | 0100011 | SH    |
| imm[11:5]             | rs2 | rs1 | 010 | imm[4:0]    | 0100011 | SW    |
| imm[11:0]             |     | rs1 | 000 | rd          | 0010011 | ADDI  |
| imm[11:0]             |     | rs1 | 010 | rd          | 0010011 | SLTI  |
| imm[11:0]             |     | rs1 | 011 | rd          | 0010011 | SLTIU |
| imm[11:0]             |     | rs1 | 100 | rd          | 0010011 | XORI  |
| imm[11:0]             |     | rs1 | 110 | rd          | 0010011 | ORI   |
| imm[11:0]             |     | rs1 | 111 | rd          | 0010011 | ANDI  |

|               |              |       |       |     |       |         |         |
|---------------|--------------|-------|-------|-----|-------|---------|---------|
| 0000000       |              | shamt | rs1   | 001 | rd    | 0010011 | SLLI    |
| 0000000       |              | shamt | rs1   | 101 | rd    | 0010011 | SRLI    |
| 0100000       |              | shamt | rs1   | 101 | rd    | 0010011 | SRAI    |
| 0000000       |              | rs2   | rs1   | 000 | rd    | 0110011 | ADD     |
| 0100000       |              | rs2   | rs1   | 000 | rd    | 0110011 | SUB     |
| 0000000       |              | rs2   | rs1   | 001 | rd    | 0110011 | SLL     |
| 0000000       |              | rs2   | rs1   | 010 | rd    | 0110011 | SLT     |
| 0000000       |              | rs2   | rs1   | 011 | rd    | 0110011 | SLTU    |
| 0000000       |              | rs2   | rs1   | 100 | rd    | 0110011 | XOR     |
| 0000000       |              | rs2   | rs1   | 101 | rd    | 0110011 | SRL     |
| 0100000       |              | rs2   | rs1   | 101 | rd    | 0110011 | SRA     |
| 0000000       |              | rs2   | rs1   | 110 | rd    | 0110011 | OR      |
| 0000000       |              | rs2   | rs1   | 111 | rd    | 0110011 | AND     |
| 0000          | pred         | succ  | 00000 | 000 | 00000 | 0001111 | FENCE   |
| 0000          | 0000         | 0000  | 00000 | 001 | 00000 | 0001111 | FENCE.I |
| 0000000000000 |              |       | 00000 | 000 | 00000 | 1110011 | ECALL   |
| 0000000000001 |              |       | 00000 | 000 | 00000 | 1110011 | EBREAK  |
| csr           | Not in CS61C |       | rs1   | 001 | rd    | 1110011 | CSRRW   |
| csr           |              |       | rs1   | 0   | rd    | 1110011 | CSRRS   |
| csr           |              |       | rs1   | 011 | rd    | 1110011 | CSRRC   |
| csr           |              |       | zimm  | 101 | rd    | 1110011 | CSRRWI  |
| csr           |              |       | zimm  | 110 | rd    | 1110011 | CSRRSI  |
| csr           |              |       | zimm  | 111 | rd    | 1110011 | CSRRCI  |

Not in CS61C

# “State” Required by RV32I ISA


Each instruction reads and updates this state during execution:

- Registers (**x0** . . **x31**)
  - Register file (or *regfile*) **Reg** holds 32 registers x 32 bits/register: **Reg**[0] . . **Reg**[31]
  - First register read specified by *rs1* field in instruction
  - Second register read specified by *rs2* field in instruction
  - Write register (destination) specified by *rd* field in instruction
  - **x0** is always 0 (writes to **Reg**[0] are ignored)
- Program Counter (**PC**)
  - Holds address of current instruction
- Memory (**MEM**)
  - Holds both instructions & data, in one 32-bit byte-addressed memory space
  - We'll use separate memories for instructions (**IMEM**) and data (**DMEM**)
    - *Later we'll replace these with instruction and data caches*
  - Instructions are read (*fetched*) from instruction memory (assume **IMEM** read-only)
  - Load/store instructions access data memory


# One-Instruction-Per-Cycle RISC-V Machine

**On every tick of the clock, the processor executes one instruction**

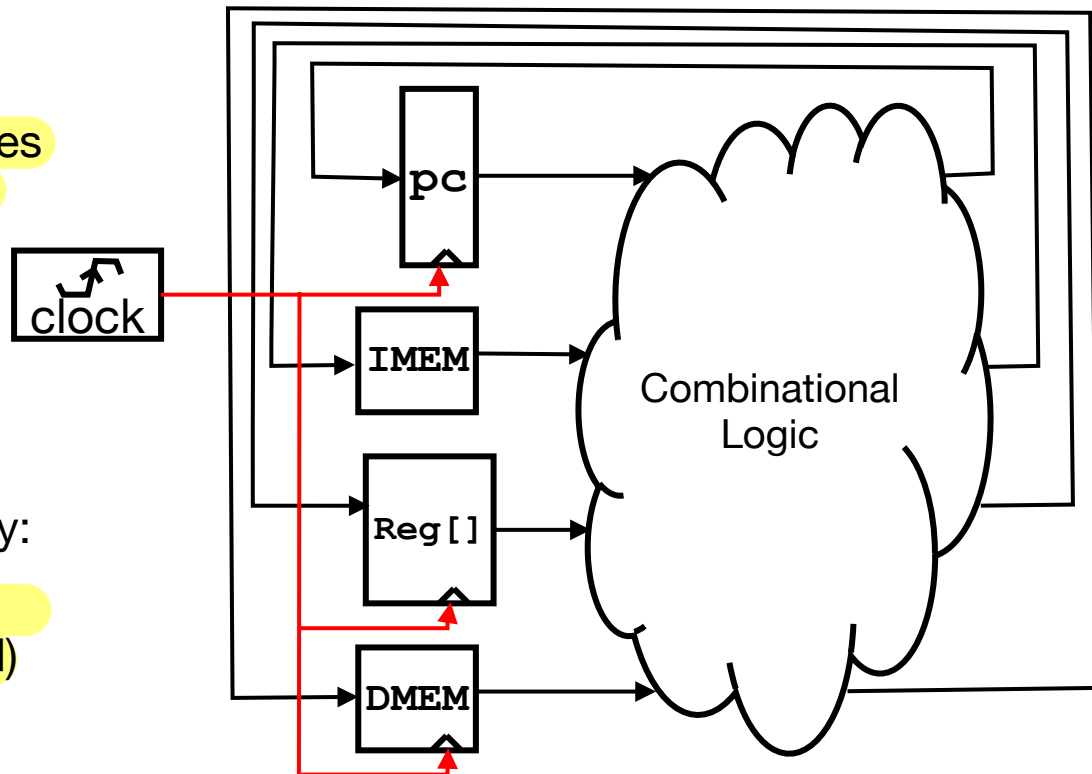1. Current state outputs drive the inputs to the combinational logic, whose outputs settles at the values of the state before the next clock edge
2. At the rising clock edge, all the state elements are updated with the combinational logic outputs, and execution moves to the next clock cycle
3. Separate instruction/data memory: For simplification, memory is asynchronous read (not clocked), but synchronous write (is clocked)



# Basic Phases of Instruction Execution

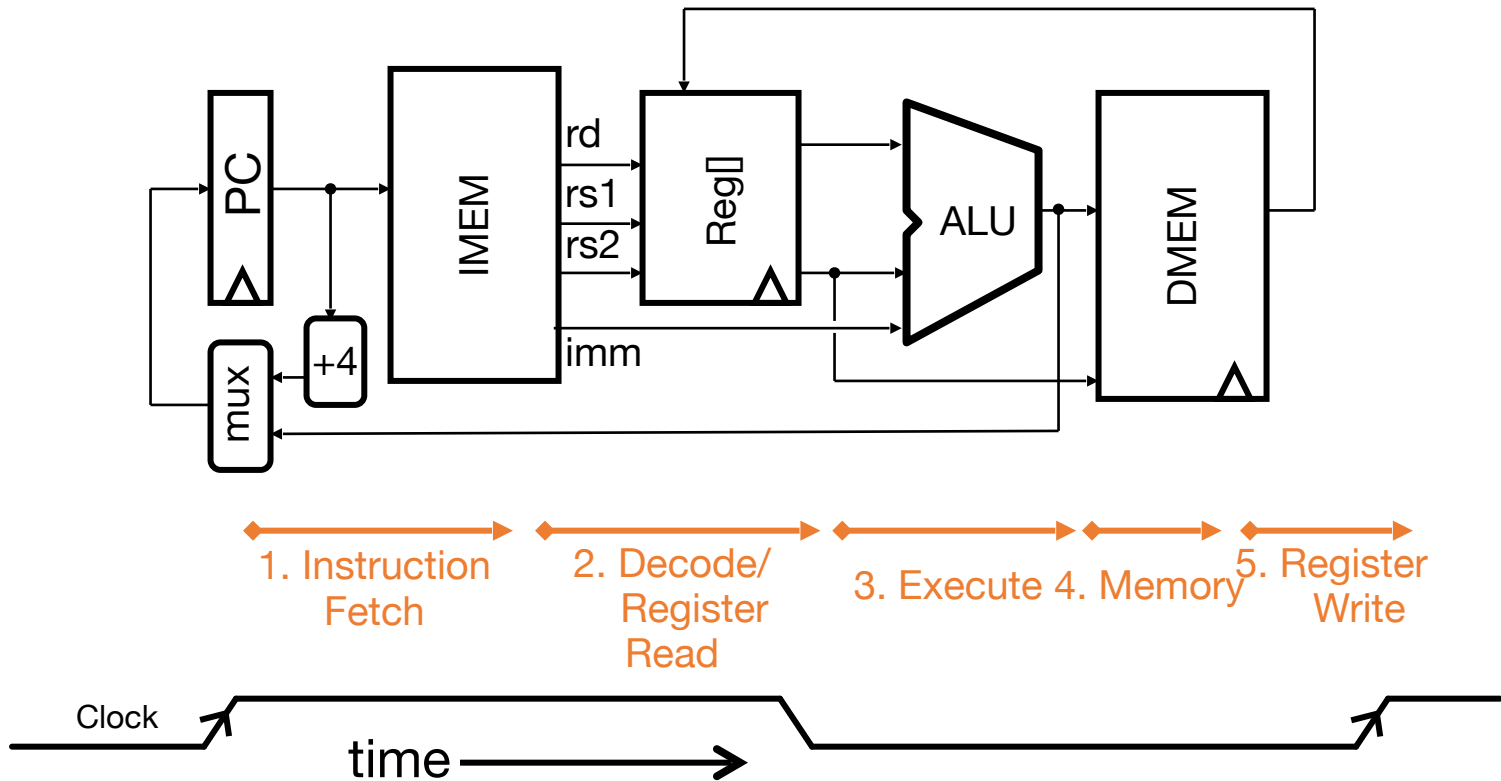

# Implementing the `add` instruction

|         |     |     |     |    |         |     |
|---------|-----|-----|-----|----|---------|-----|
| 0000000 | rs2 | rs1 | 000 | rd | 0110011 | ADD |
|---------|-----|-----|-----|----|---------|-----|


- Instruction makes two changes to machine's state:

**$\text{Reg}[\text{rd}] = \text{Reg}[\text{rs1}] + \text{Reg}[\text{rs2}]$**


**$\text{PC} = \text{PC} + 4$**



# Datapath for add

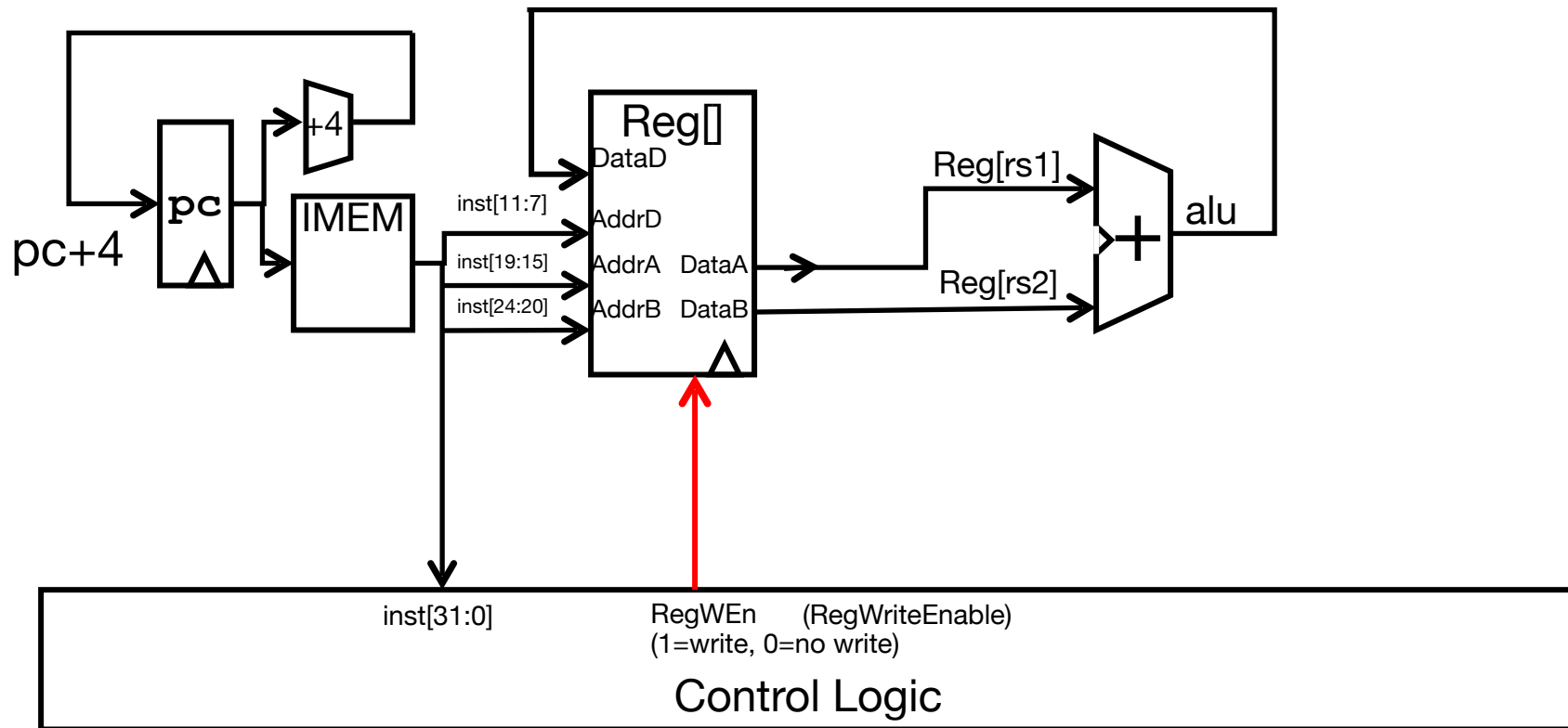

# Timing Diagram for add

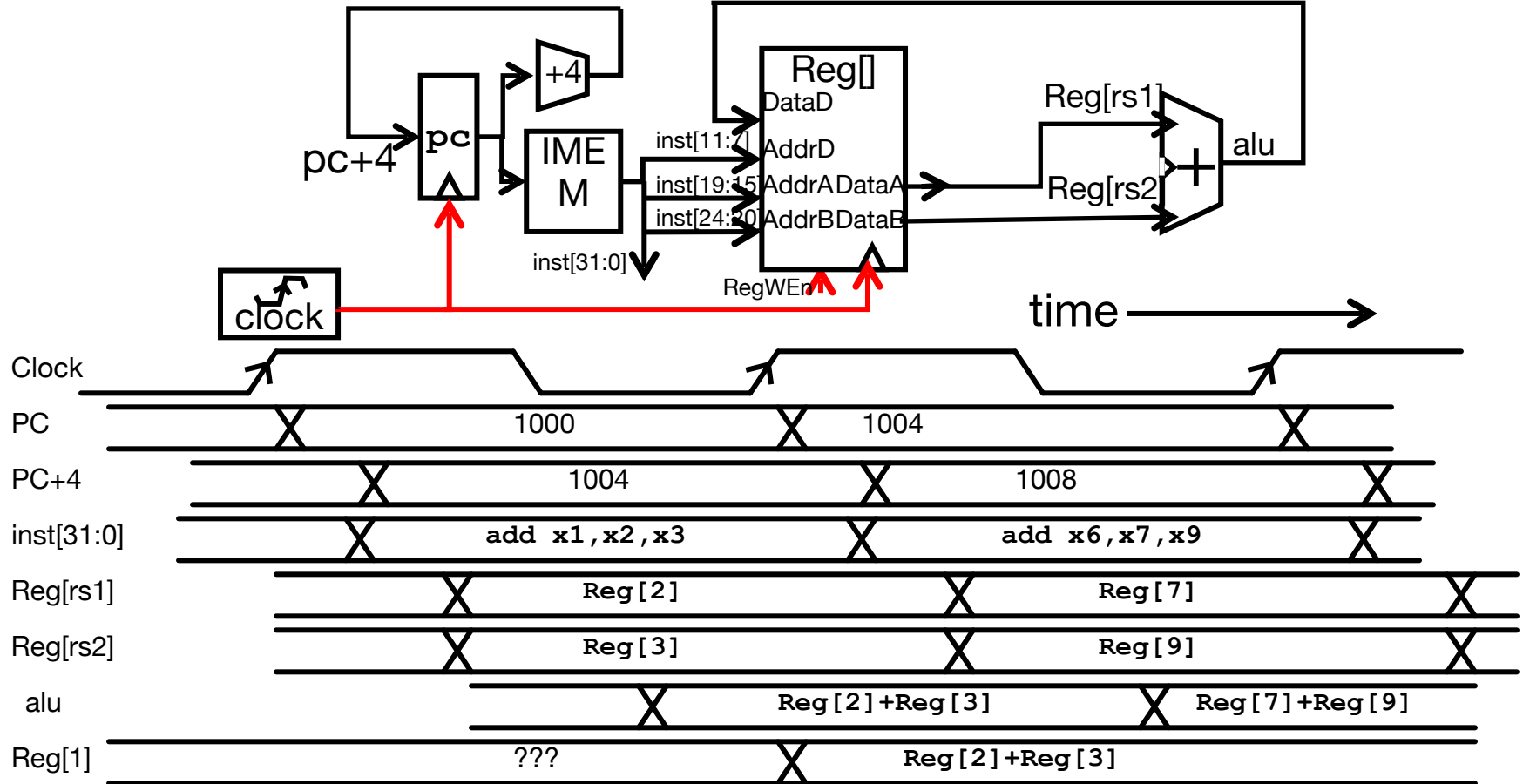


# Implementing the **sub** instruction

|         |     |     |     |    |         |     |
|---------|-----|-----|-----|----|---------|-----|
| 0000000 | rs2 | rs1 | 000 | rd | 0110011 | ADD |
| 0100000 | rs2 | rs1 | 000 | rd | 0110011 | SUB |

- Almost the same as **add**, except now have to subtract operands instead of adding them
- **inst[30]** selects between add and subtract

# Datapath for add/sub

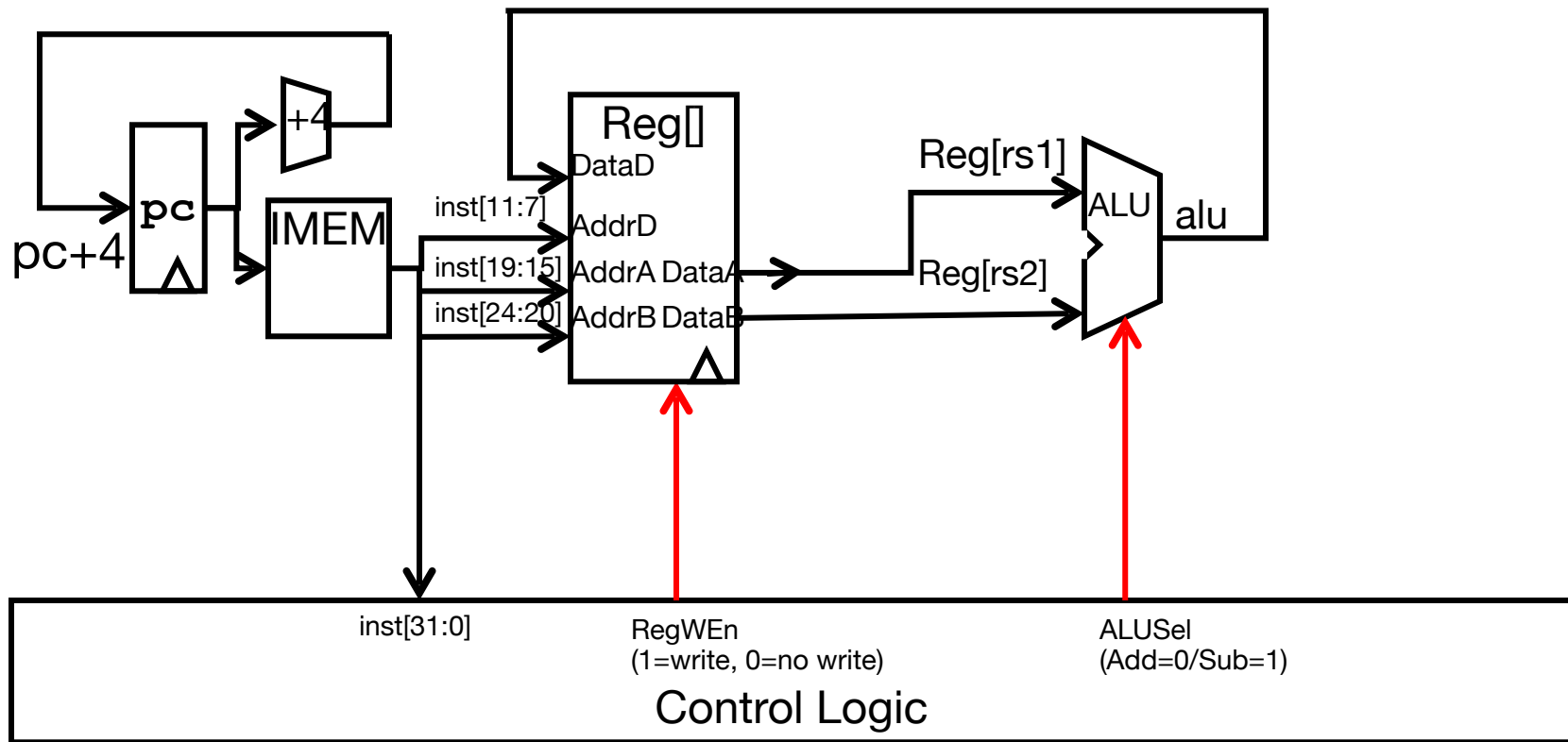



# Implementing other R-Format instructions

|         |     |     |     |    |         |      |
|---------|-----|-----|-----|----|---------|------|
| 0000000 | rs2 | rs1 | 000 | rd | 0110011 | ADD  |
| 0100000 | rs2 | rs1 | 000 | rd | 0110011 | SUB  |
| 0000000 | rs2 | rs1 | 001 | rd | 0110011 | SLL  |
| 0000000 | rs2 | rs1 | 010 | rd | 0110011 | SLT  |
| 0000000 | rs2 | rs1 | 011 | rd | 0110011 | SLTU |
| 0000000 | rs2 | rs1 | 100 | rd | 0110011 | XOR  |
| 0000000 | rs2 | rs1 | 101 | rd | 0110011 | SRL  |
| 0100000 | rs2 | rs1 | 101 | rd | 0110011 | SRA  |
| 0000000 | rs2 | rs1 | 110 | rd | 0110011 | OR   |
| 0000000 | rs2 | rs1 | 111 | rd | 0110011 | AND  |


# Implementing the **addi** instruction

- RISC-V Assembly Instruction:


**addi    x15, x1, -50**

  

# Datapath for add/sub


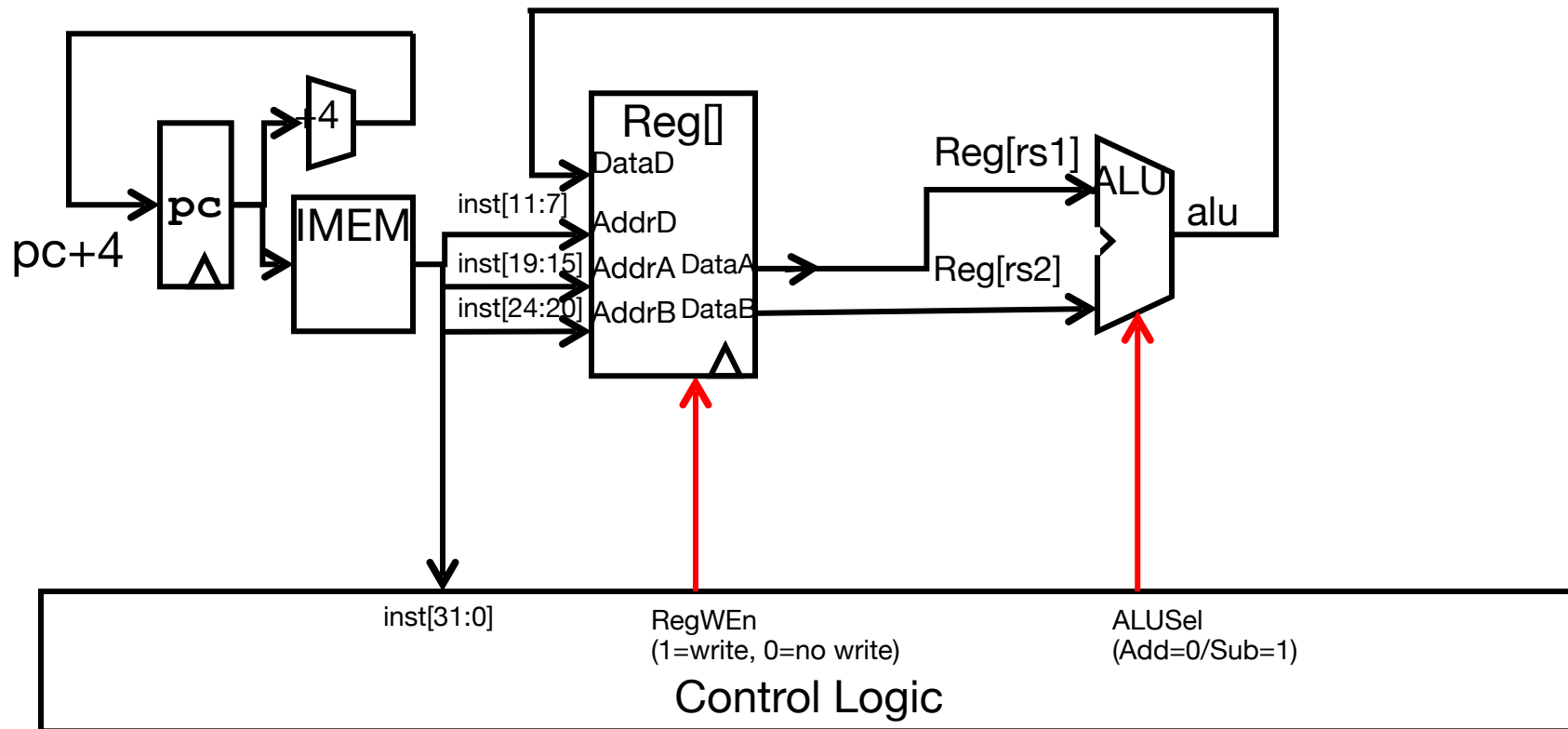


# Adding `addi` to datapath

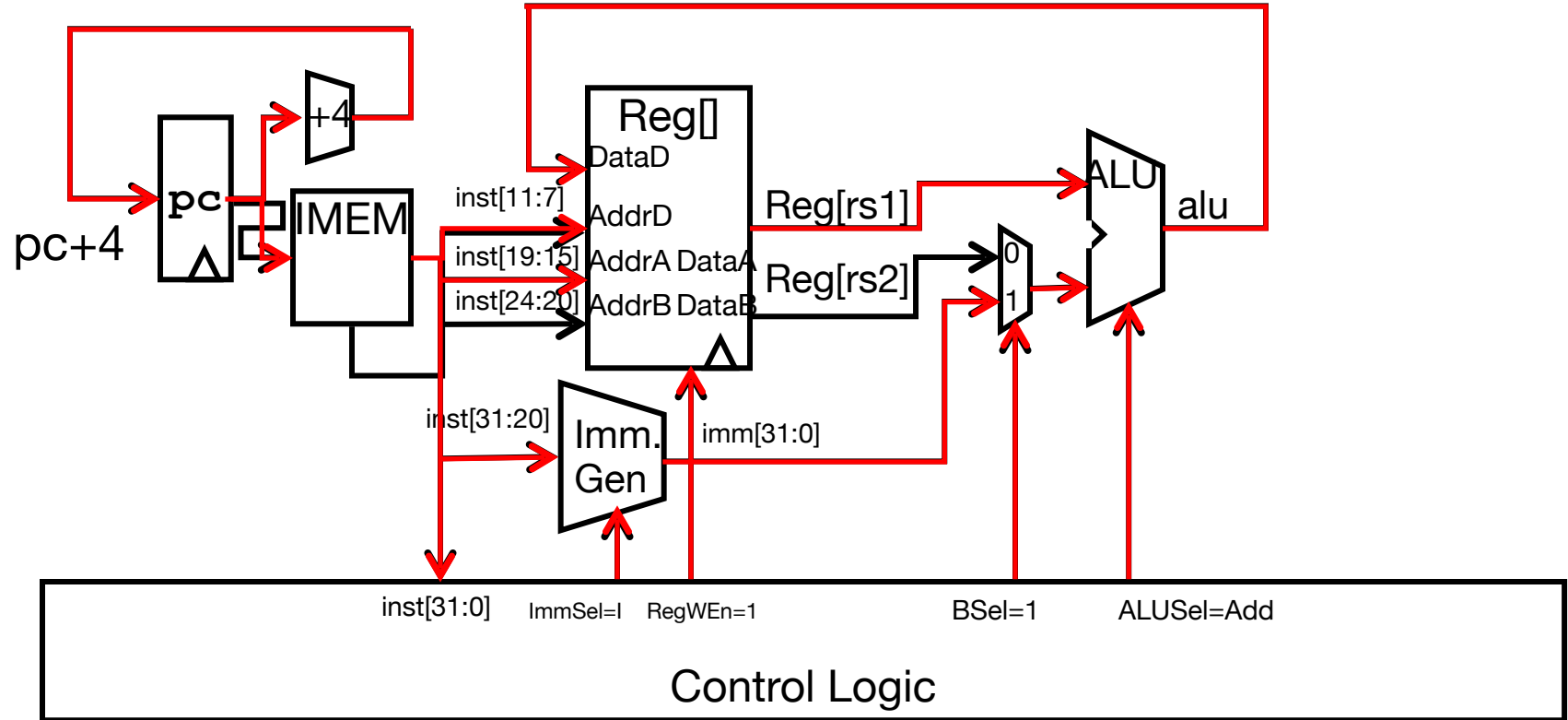




# I-Format immediates

  

- High 12 bits of instruction (**inst[31:20]**) copied to low 12 bits of immediate (**imm[11:0]**)
- Immediate is sign-extended by copying value of **inst[31]** to fill the upper 20 bits of the immediate value (**imm[31:12]**)

# Adding `addi` to datapath


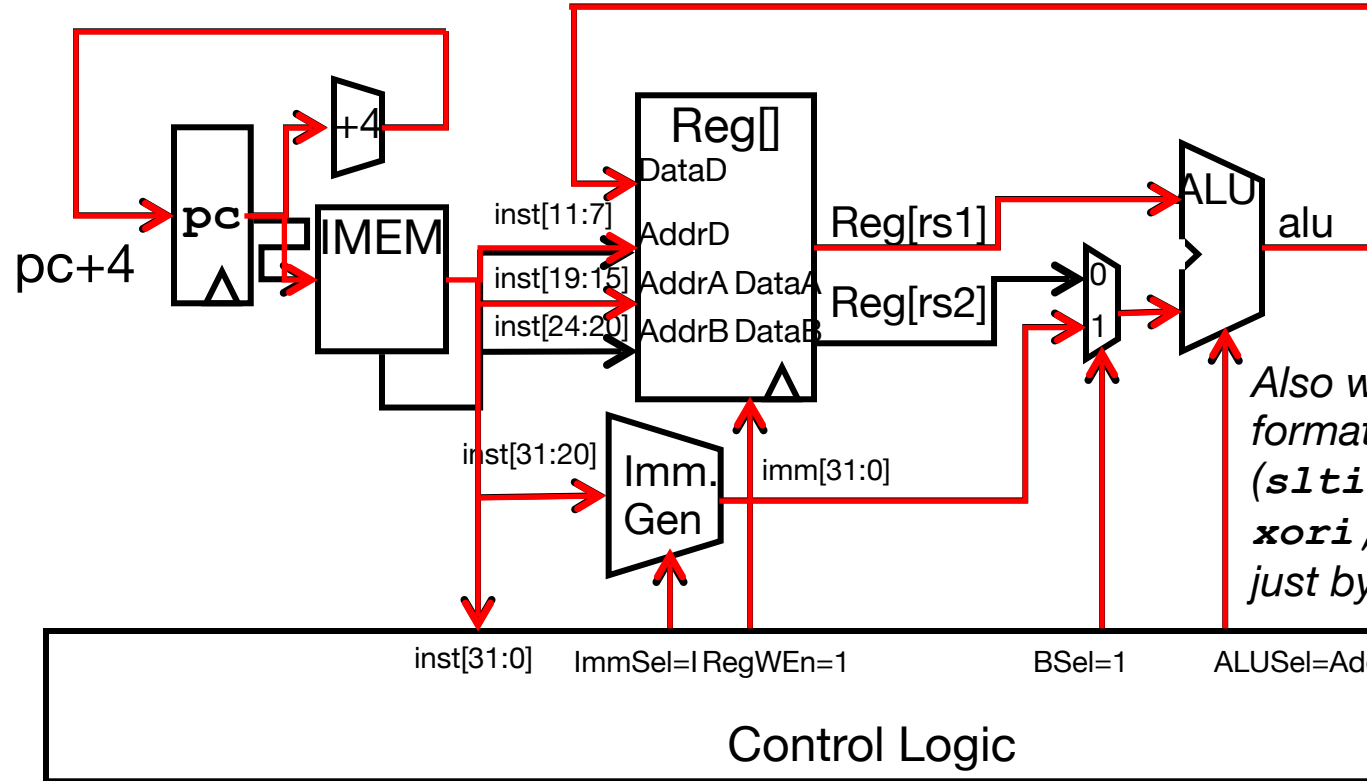


*Also works for all other I-format arithmetic instruction (`slti`, `sltiu`, `andi`, `ori`, `xori`, `slli`, `srli`, `srai`) just by changing `ALUSel`*


# Implementing Load Word instruction

- RISC-V Assembly Instruction:


**lw x14, 8(x2)**

  


# Adding **addi** to datapath

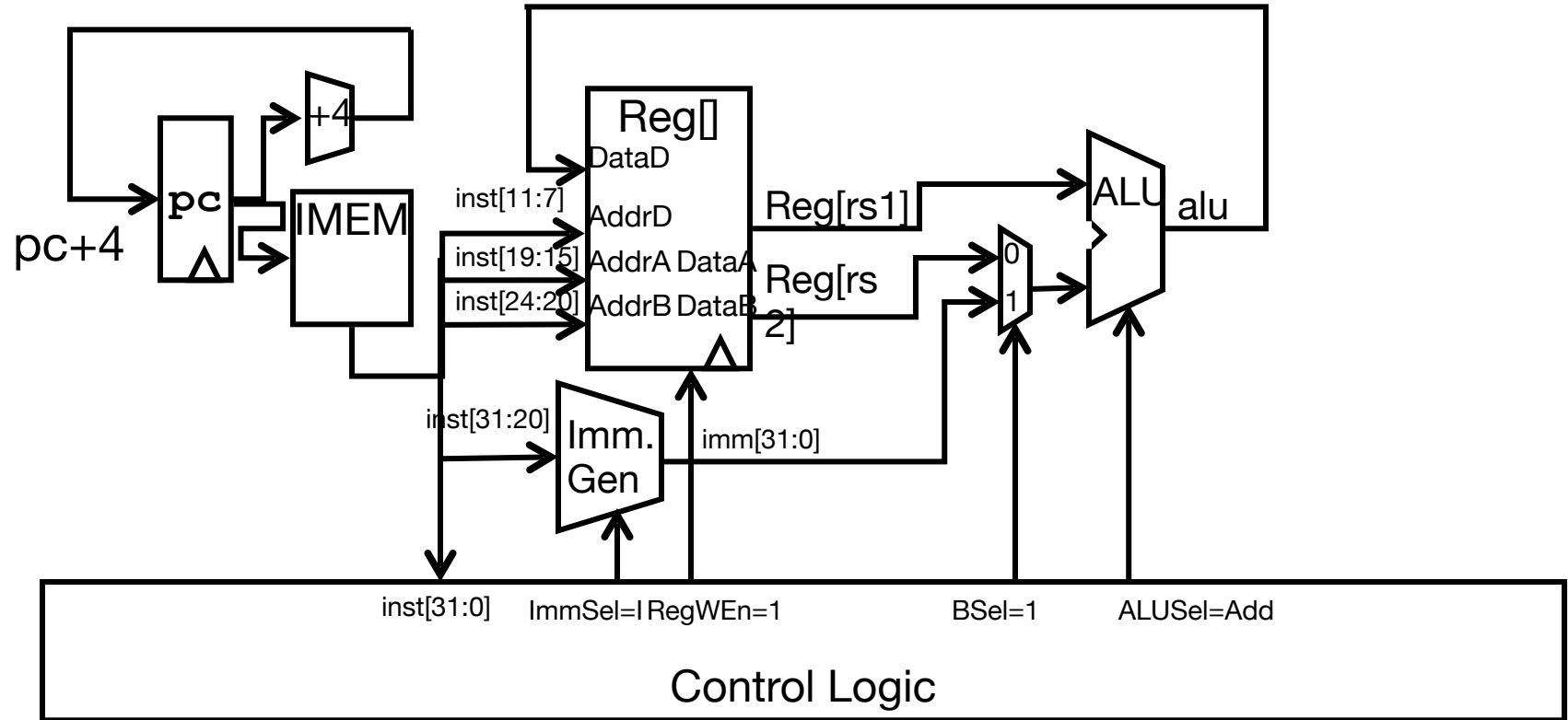

# Adding 1w to datapath

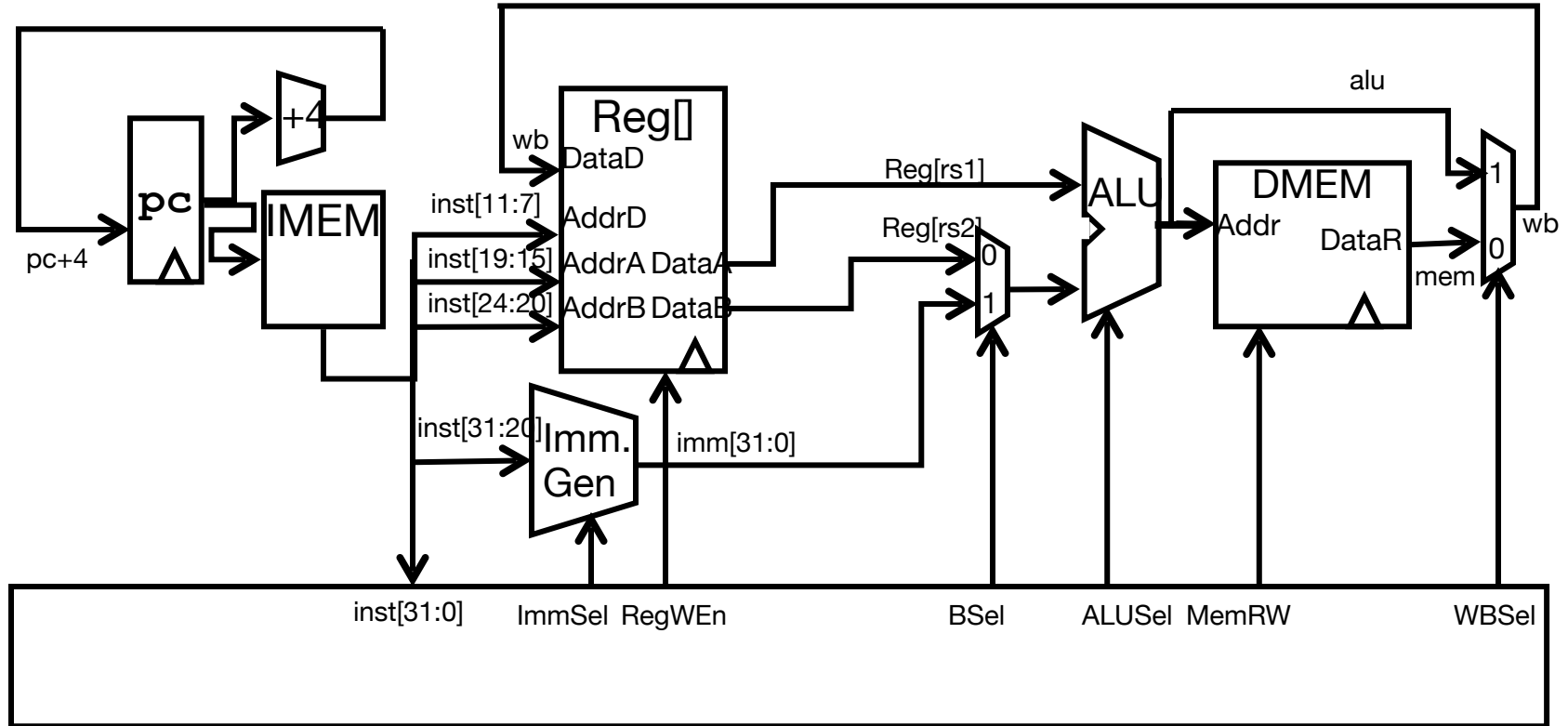

# Adding 1w to datapath

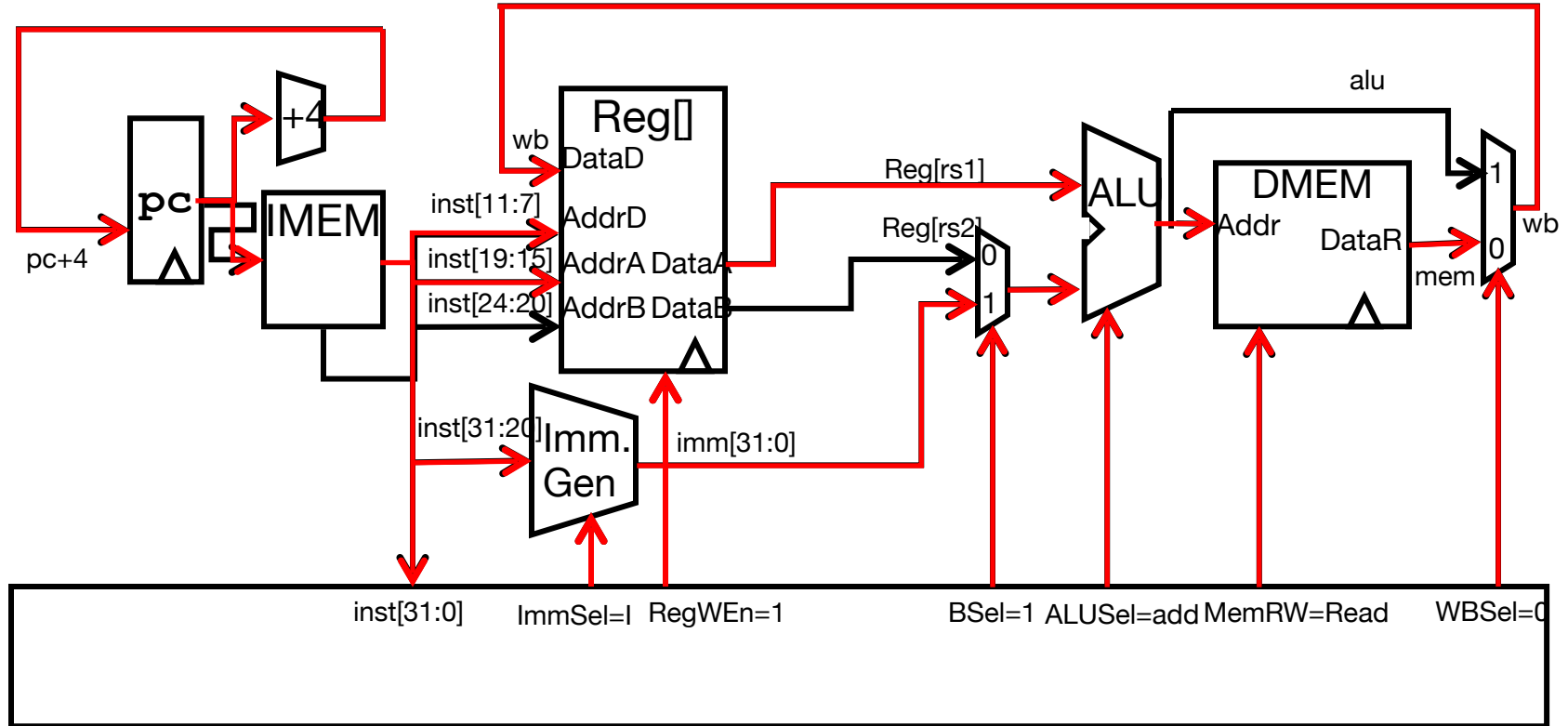

# All RV32 Load Instructions

|           |     |     |    |         |     |
|-----------|-----|-----|----|---------|-----|
| imm[11:0] | rs1 | 000 | rd | 0000011 | LB  |
| imm[11:0] | rs1 | 001 | rd | 0000011 | LH  |
| imm[11:0] | rs1 | 010 | rd | 0000011 | LW  |
| imm[11:0] | rs1 | 100 | rd | 0000011 | LBU |
| imm[11:0] | rs1 | 101 | rd | 0000011 | LHU |


↑  
funct3 field encodes size  
and signedness of load  
data

- Supporting the narrower loads requires additional circuits to extract the correct byte/halfword from the value loaded from memory, and sign- or zero-extend the result to 32 bits before writing back to register file.


# Implementing Store Word instruction

- RISC-V Assembly Instruction:

**sw x14, 8(x2)**

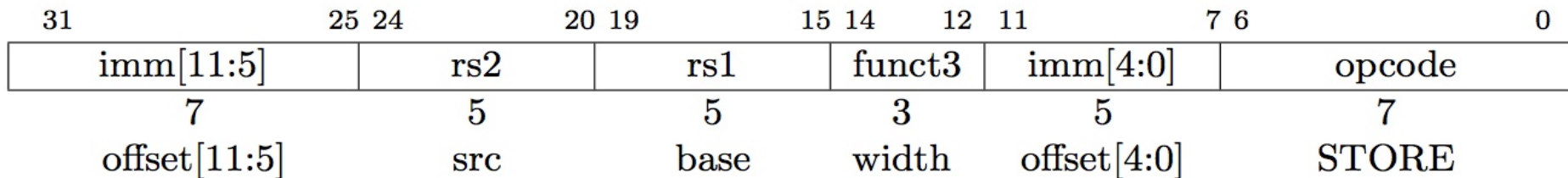


offset[11:5] = 0      rs2=14      rs1=2      SW      offset[4:0] = 8      STORE

 


combined 12-bit offset = 8




# Adding 1w to datapath

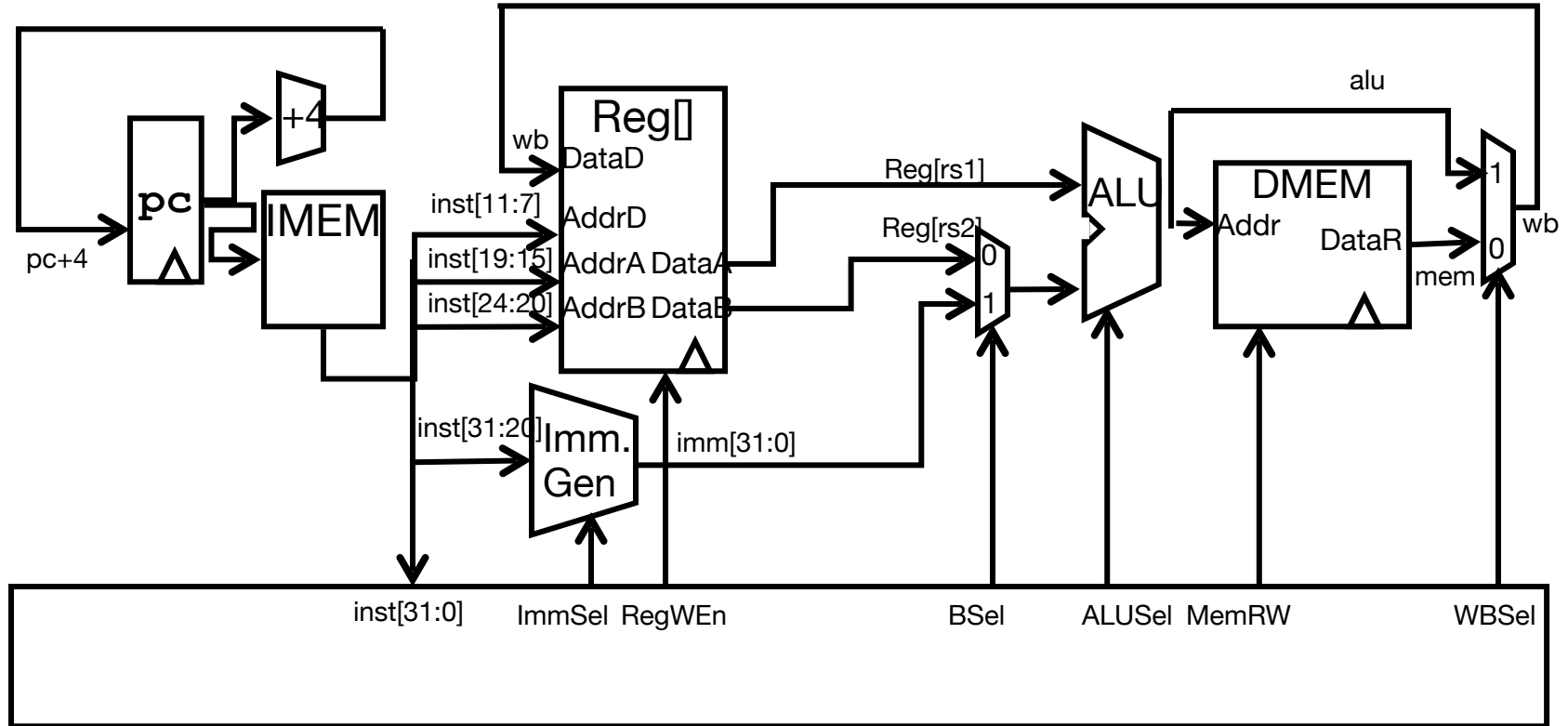



# Adding **sw** to datapath

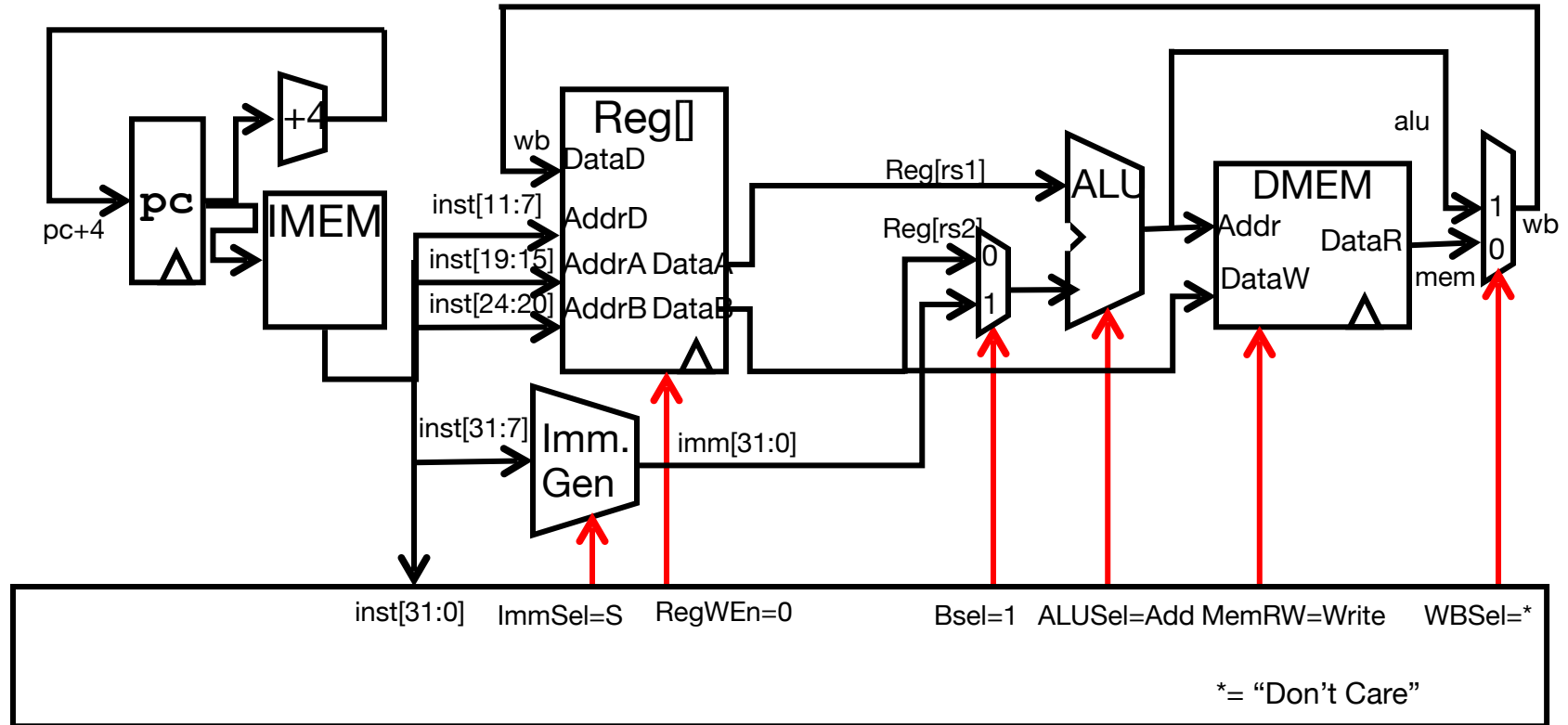

# Adding **sw** to datapath

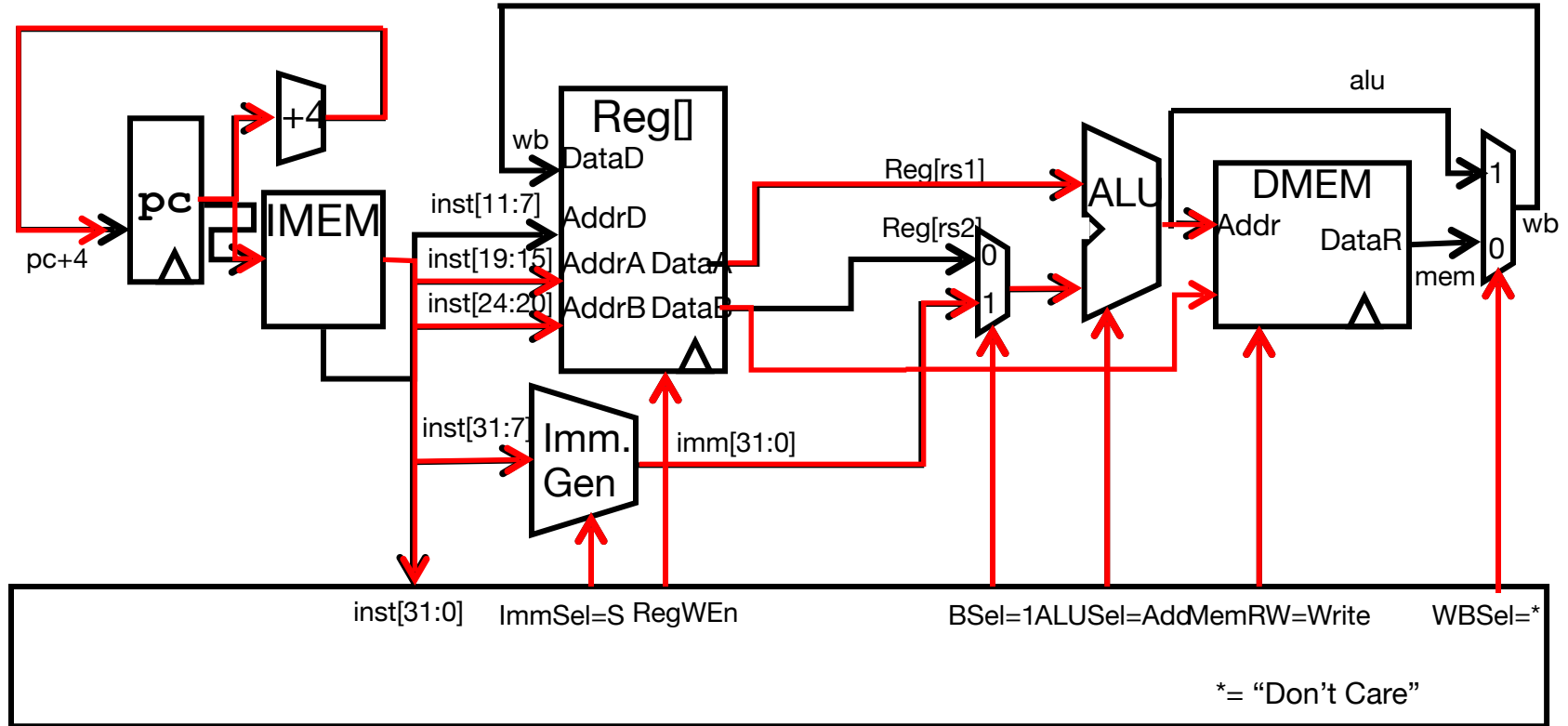


# I-Format immediates

 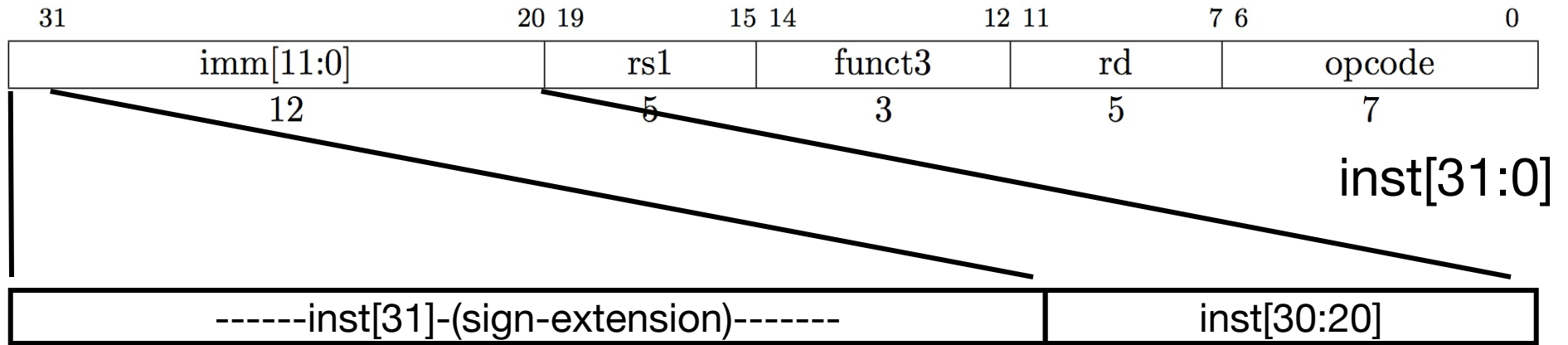


- High 12 bits of instruction (inst[31:20]) copied to low 12 bits of immediate (imm[11:0])
- Immediate is sign-extended by copying value of inst[31] to fill the upper 20 bits of the immediate value (imm[31:12])

# I & S Immediate Generator

 


- Just need a 5-bit mux to select between two positions where low five bits of immediate can reside in instruction
- Other bits in immediate are wired to fixed positions in instruction

# Implementing Branches

 


- B-format is mostly same as S-Format, with two register sources (rs1/rs2) and a 12-bit immediate
- But now immediate represents values -4096 to +4094 in 2-byte increments
- The 12 immediate bits encode *even* 13-bit signed byte offsets (lowest bit of offset is always zero, so no need to store it)

# Adding **sw** to datapath

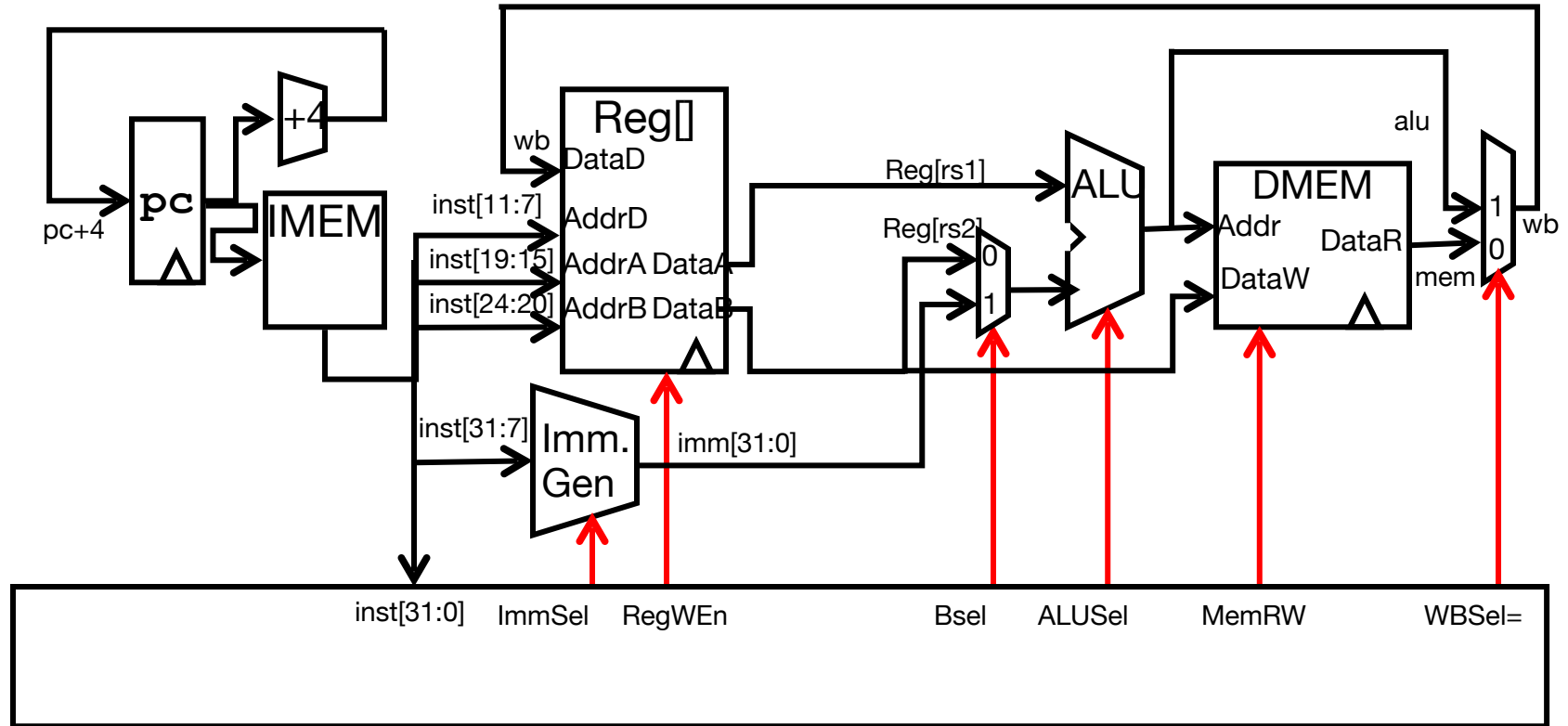


# Adding branches to datapath

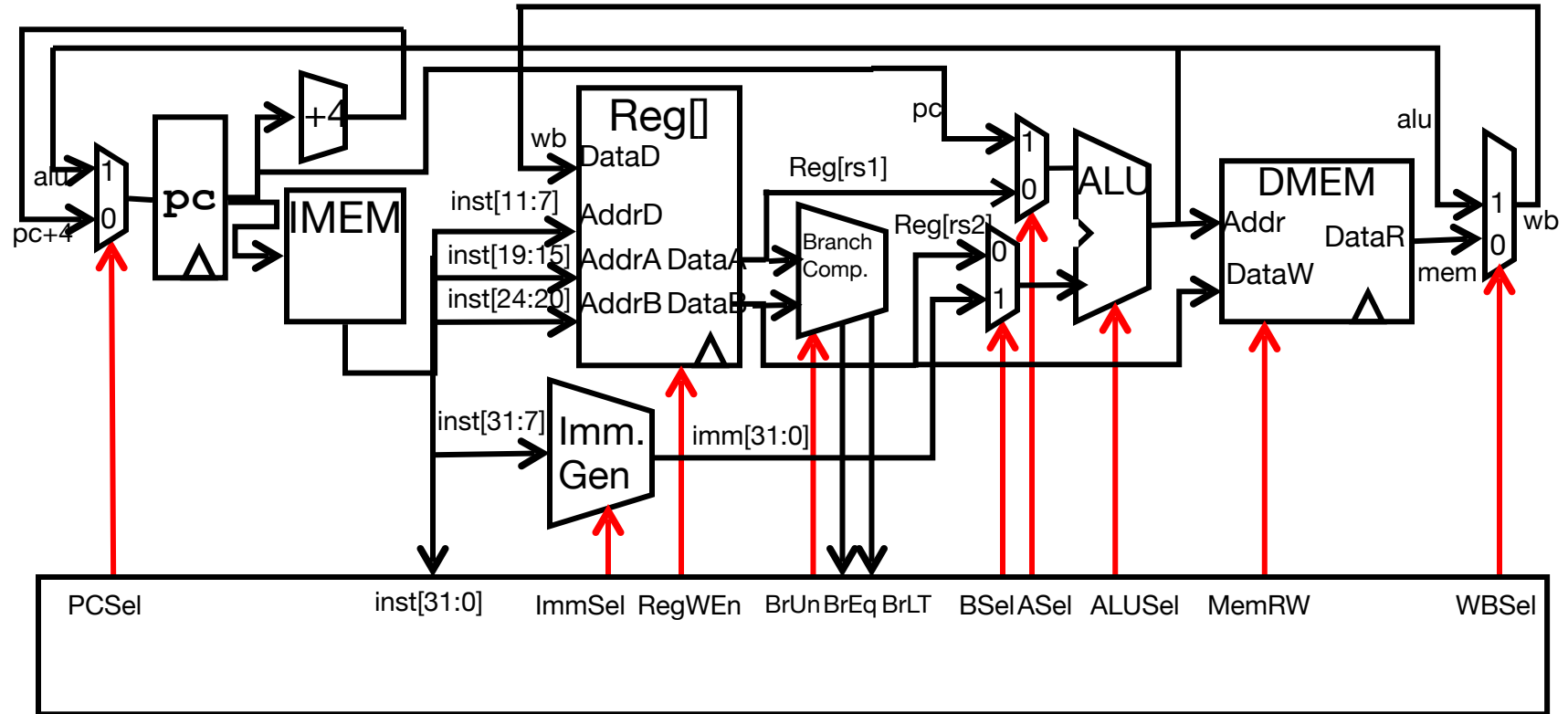




# Adding branches to datapath

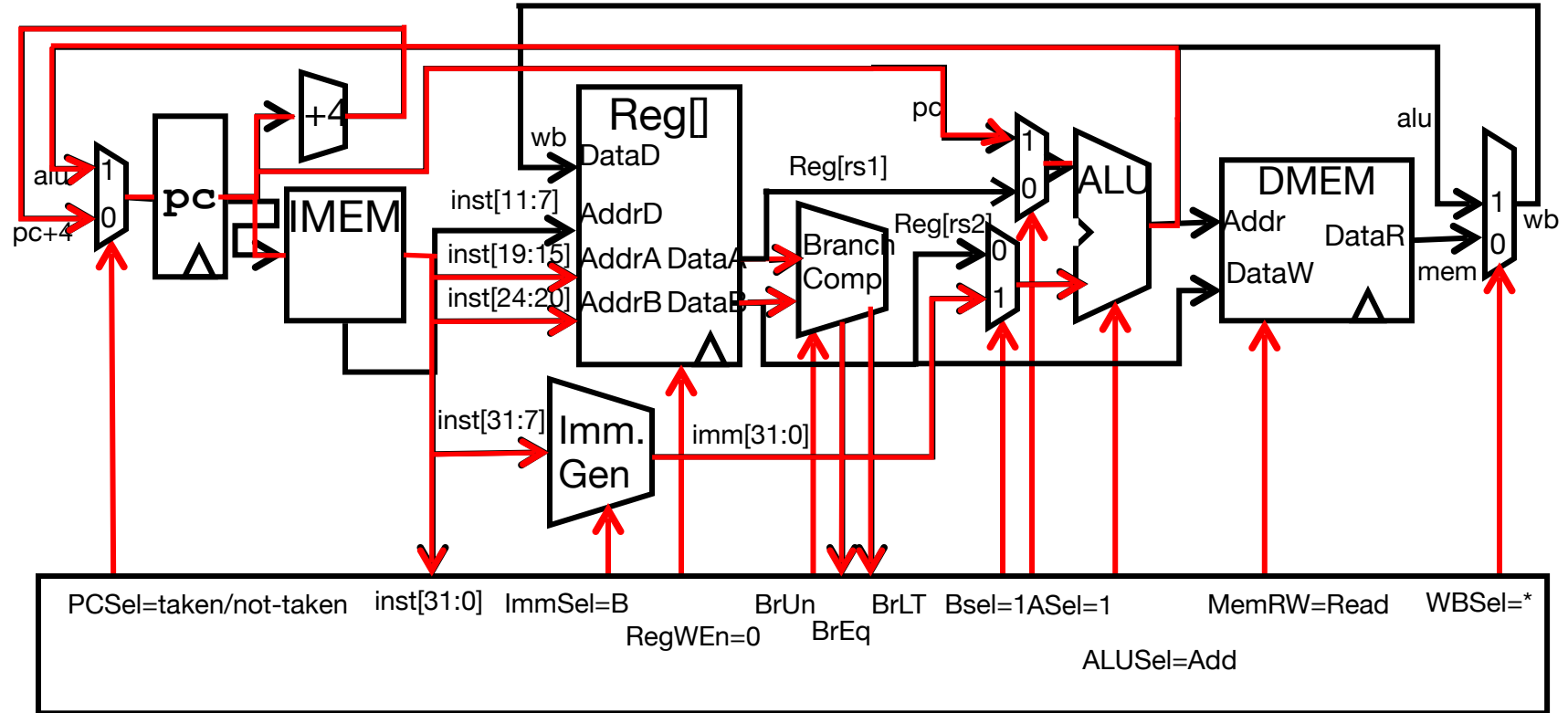

 
# Branch Comparator

- $\text{BrEq} = 1$ , if  $A=B$
- $\text{BrLT} = 1$ , if  $A < B$
- $\text{BrUn} = 1$  selects unsigned comparison for  $\text{BrLT}$ , 0=signed
- BGE branch:  $A \geq B$ , if  $\neg(A < B)$



 
# Implementing **JALR** Instruction (I-Format)




- Sets  $PC = \text{Reg}[\text{rs1}] + \text{immediate}$
- Uses same immediates as arithmetic and loads
  - **no** multiplication by 2 bytes


# Adding branches to datapath

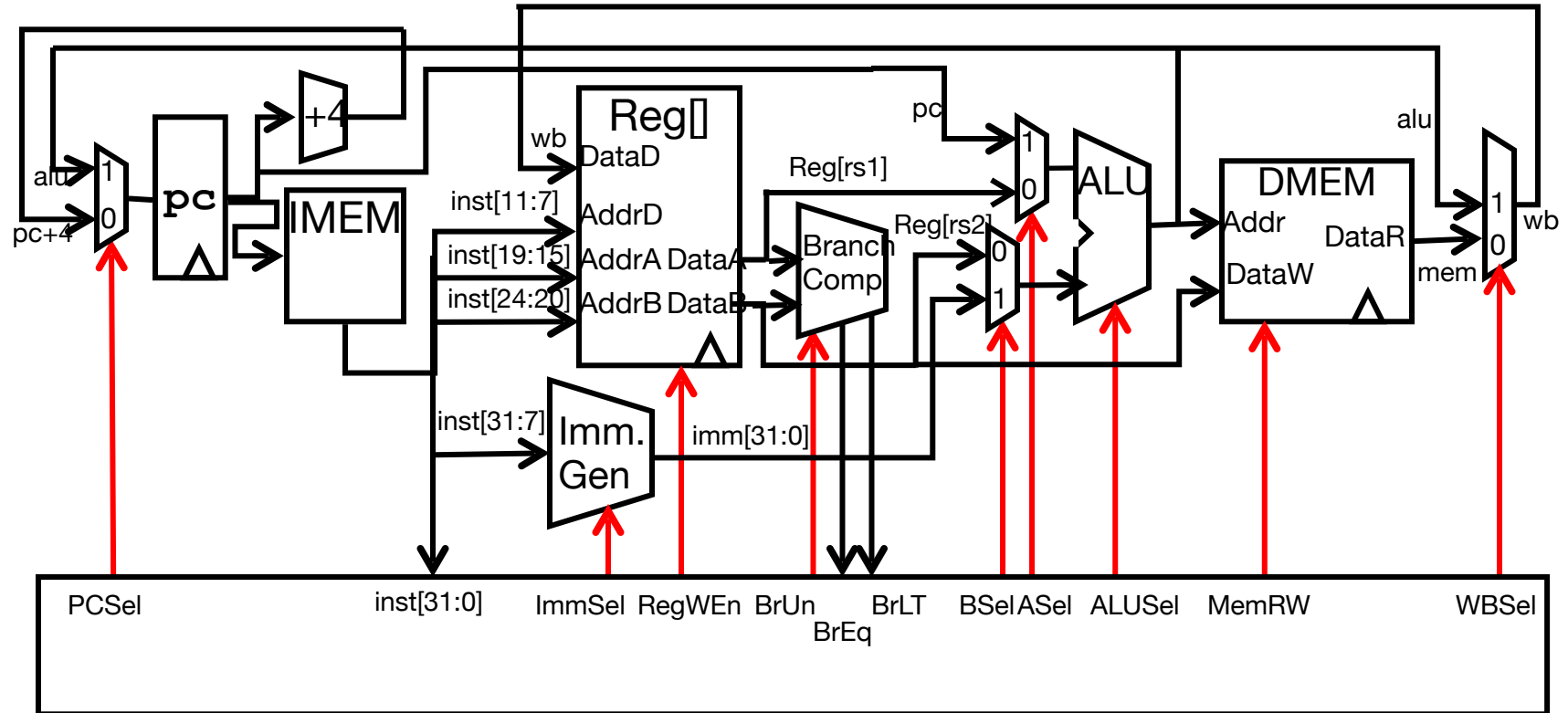


# Adding jalr to datapath

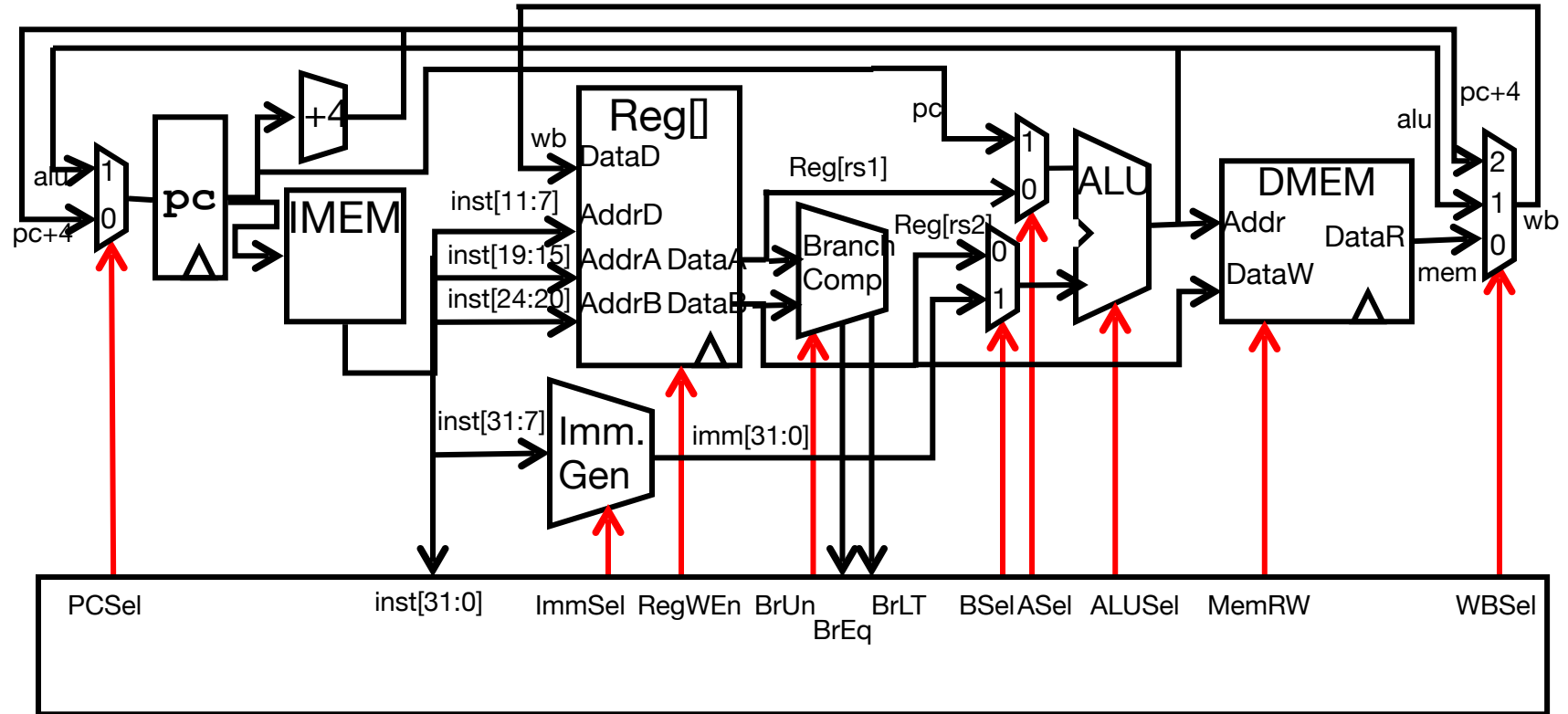

# Adding jalr to datapath

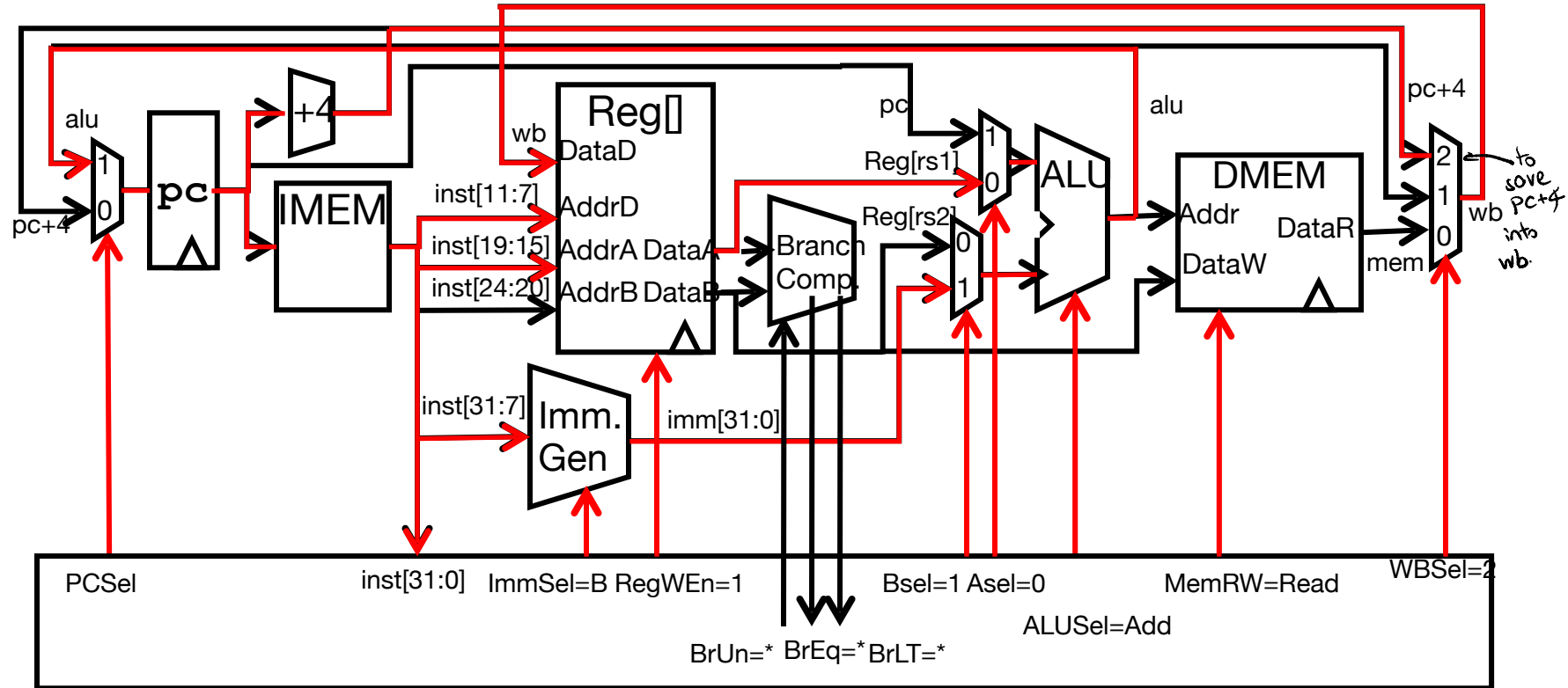


# Implementing jal Instruction

 


- JAL saves PC+4 in Reg[rd] (the return address)
- Set PC = PC + offset (PC-relative jump)
- Target somewhere within  $\pm 2^{19}$  locations, 2 bytes apart
  - $\pm 2^{18}$  32-bit instructions
- Immediate encoding optimized similarly to branch instruction to reduce hardware cost

# Adding jal to datapath

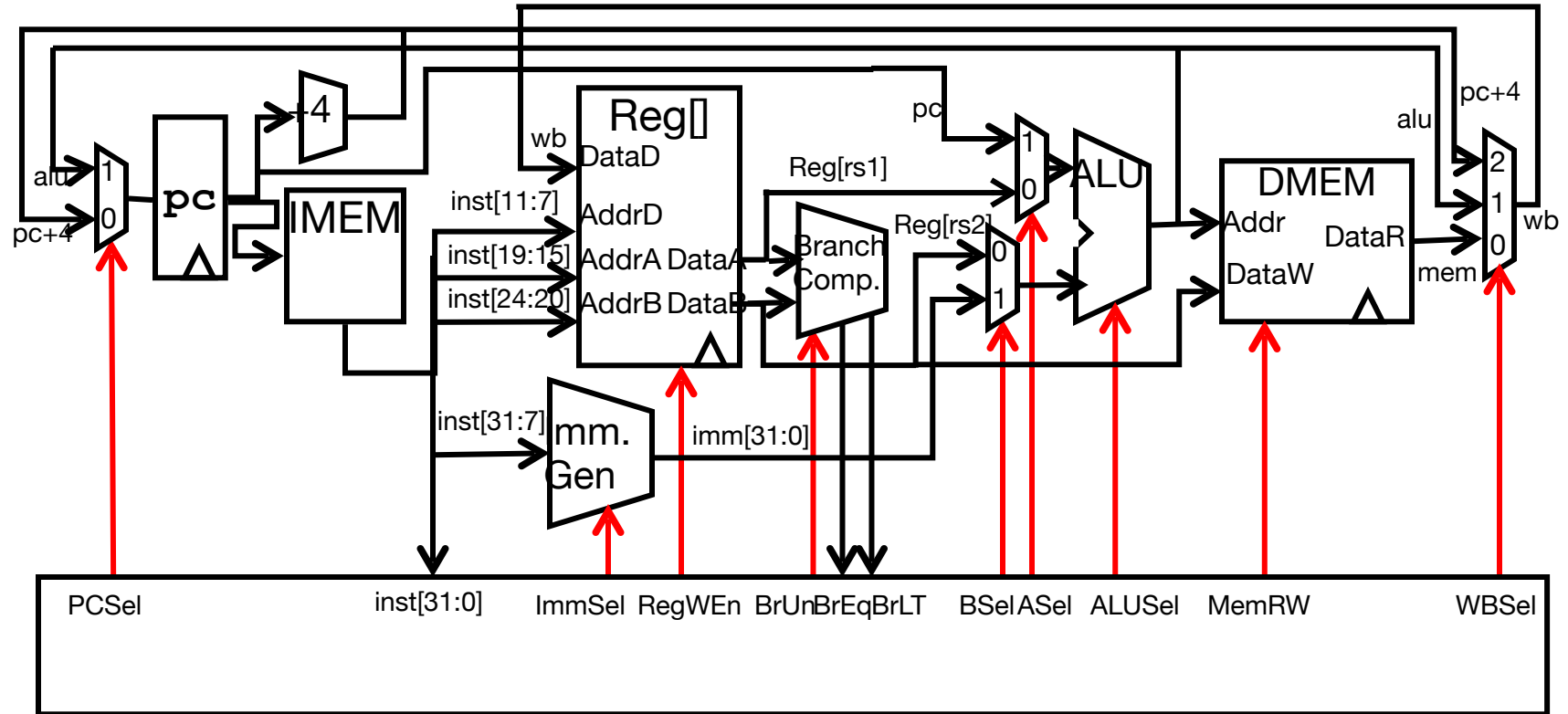




# Adding jal to datapath

 

# Single-Cycle RISC-V RV32I Datapath

 

# And in Conclusion, ...

- Universal datapath
  - Capable of executing all RISC-V instructions in one cycle each
  - datapath is the “union” of all the units used by all the instructions. Muxes provide the options.
  - Not all units (hardware) used by all instructions
- 5 Phases of execution
  - IF, ID, EX, MEM, WB
  - Not all instructions are active in all phases
- Controller specifies how to execute instructions